EE271 Sp23
April 7, 2023
Lab 1 Submission

Name: **Aaryan Pawar**

Q1: A simple, correct explanation of what the mux4_1 circuit does

The mux4_1 circuit routes one of the four signals (i00, i01, i10, i11) inputted to the circuit based on the two input bits (sel0, sel1).

Q2: The value of the signal (TRUE or FALSE) that makes the LEDR's light up TRUE

Q3: The position of the slider switches that cause them to output TRUE (we will assume up/down are referenced as if you have the board positioned so the switches are closer to you)
Flicking the switch up outputs TRUE, flicking down outputs FALSE

Q4: The position of the pushbuttons that cause them to output TRUE
Up -> TRUE
Down -> FALSE

Your demo day and time: Friday, 11:30
Who you demoed with: Jason